

## EE6044 Advanced Analog IC Design – Homework 3

### Question 1

1.

You have been tasked with designing a front-end preamplifier for the sensor interface of an ultra low-power wireless sensor node. An example of such a sensor is a piezoelectric device which could be used to measure industrial motor vibrations for fault detection. The specifications you have been given for this application are as follows:

Table 1.1. Front-end Preamplifier Specification

Parameter	Specification
$A_v$	$> 50$
$f_u$	$50MHz$
$v_{out}$	$> 600mV_{p-to-p}$
$V_{OUT,Q}$	$0.6V$
$V_{DD}$	$1.2V$
$C_L$	$2pF$
$\overline{v}_n^{in}$	$\leq 250nV/\sqrt{Hz}$
$I_{bias}$	$4\mu A$

For simplicity, the architecture you must use is the Common Source Amplifier with Active Load, shown in Figure 1:

 


Figure 1: PMOS Input Common Source (CS) Amplifier with Active Load

- Derive an expression for the small signal gain of the gain stage. **[5 marks]**
- As a rule of thumb we usually set  $f_T \geq 10 * f_u$ . Derive an expression relating  $f_T$ ,  $g_m/I_D$  and Area ( $WL$ ). **[5 marks]**
- From the CS circuit small signal model, derive an expression for the unity gain frequency  $f_u$  considering  $g_m/I_D$  of M1, the current of M1  $M * I_{bias}$ ,  $C_{dd}^1$ ,  $C_{dd}^2$ , and  $C_L$ . **[5 marks]**
- What is your initial estimate for  $g_m/I_D$  ratio for each transistor state why?. (Hint: low power operation of the gain stage is the design goal, balance this with the maximum  $V_{DSAT}$  that can be used for the load device M2.) **[5 marks]**

## Question 2

The design is to be carried out on the Skywater 0.13 $\mu m$  process. In the following questions, assume the following:  $V_{DD} = 1.2V$ ,  $L = 0.2\mu m$ ,  $\gamma = 0.85$  for all transistors. For this question use python and the lookup functions to calculate your answers. Note that the  $g_m/I_D$  script assumes  $L$  &  $W$  in  $\mu m$ , all other quantities in the usual units. Remember  $I_{bias} = 4\mu A$  and  $V_{out}^Q = \frac{V_{DD}}{2} V$ .

- Sweep the device length of M1 to see if the minimum gain spec of 50 can be achieved. (Hint as a simplification use the equation from 1(a) and set  $g_{ds2} = 0.125 * g_{ds1}$ ). Using the look\_up ('GM\_GDS' ) Produce a plot of gain versus  $L_1$  to show the minimum length required to achieve the gain. Plot the gain for the estimated  $g_m/I_D$  from 1(a) and repeat the plot for four other  $g_m/I_D$  ratios. **[10 marks]**

- (b) Setting the constraint  $f_T \geq 10 * f_u$  use the `look_up("GM_CGG")` function to check that the  $L_1$  and  $g_m/I_D$  values from 2(a) satisfy this constraint. **[6 marks]**
- (c) Take the expression for  $f_U$  from 1(c) and initially ignoring the parasitic capacitors  $C_{dd}^1$  and  $C_{dd}^2$  using the  $L_1$  and  $g_m/I_D$  values that satisfy 2(b) find the minimum  $M * I_{Bias}$  where M is an integer that can achieve  $f_U = 10MHz$ . (Hint: solve the equation for M ). Calculate the value of  $g_{m1}$ . **[8 marks]**
- (d) Using the  $g_m/I_D$  values for M2 from 1(d) and the current from 2(c) find the values of  $L_2$  and  $W_2$  that achieve the requirement from 2(a) that  $g_{ds2} = 0.125 \times g_{ds1}$ . (Hint use the (lookup 'ID\_W') to find  $W_2$  and the `lookup("GM_GDS")` function with the  $g_m/I_D$  to find  $L_2$ . **[6 marks]**

### Question 3

- (a) From the value of  $\gamma$  given above, and the  $g_m$  values in 3(a), calculate the thermal spot noise current of each of the transistors. Refer this to the gate of the input transistor  $M_n^{M1}$  to obtain  $\bar{v}_n^{in}$ . Does this meet spec? **[9 marks]**
- (b) Use the `lookupVGS` function to find the  $V_{GS}^{M1}$  and  $V_{GS}^{M2}$ . **[5 marks]**
- (c) Using the equation from 1 (c) and the `lookup` function to calculate the  $C_{db}$  of  $M_n^{M2}$  and  $M_p^{M1}$ . (`Cdd_M1 = PCH.look_up( 'CDD', VGS=Vgs_M1,` Along with the  $g_{m1}$  values obtained in Q2 (c), check that the requirement  $f_U = 50MHz$  is still satisfied. **[7 marks]**
- (d) If you are designing a current mirror active load would you use devices biased in weak inversion or strong inversion. Explain. **[4 marks]**

### Question 4

Draw up your design in Cadence using the W and  $V_{BIAS}$  values calculated previously. Use the following analysis to validate the performance of your design:

- (a) Perform DC Operating Point analysis to confirm  $I_D^{M1}$ ,  $V_{out}^Q$ ,  $g_m I_D$ ,  $g_{ds}$  and  $C_{db}$  of all transistors. Confirm the headroom requirement by performing a DC sweep of the input  $v_{in}$ . **[7 marks]**
- (b) Perform AC analysis to confirm the bandwidth of the circuit. **[8 marks]**
- (c) Perform 'noise' analysis to confirm the thermal spot noise floor of the circuit. Plot the 'input noise' parameter from Direct Plot options. Ignore low frequency flicker noise effects. **[10 marks]**